

Jawaharlal Nehru Govt. Engineering College Sundernagar, Mandi (H.P.)

Course Name: Basic Electrical Engg.

Course Code: EE-111

Examination: 2nd periodical Examination

Scheme: NEP

Branch: ECE, CE, CSE

Semester: 1st

Question Paper for 2nd Periodical Examinations (Nov, 2025)

Time: One and a half hours

Max. Marks: 30

CO	Course Outcomes
CO1	Recalling Basic Electrical and magnetic laws
CO2	Remembering Steady State analysis of DC circuits
CO3	Understanding AC Single phase & Three phase Circuits
CO4	Solving complex AC, DC circuits
CO5	Explaining various concepts of Electrical machines

Q No	Questions	Marks	Targeted CO	Targeted KL
1.a	Draw the diagram of shell type transformer?	1	5	2
1.b	What is done to minimize eddy current losses?	1	5	1
1.c	Define Transient Response?	1	5	1
1.d	What is working principle of transformer?	1	2	2
1.e	What is difference between phase & line voltage?	1	4	1
2.	What is ideal transformer? Also Derive EMF Equation of transformer?	5	5	2
4.	Find the transient response of series RL circuit for charging and discharging?	10	2	2
5.	Explain the power by two wattmeter method in a 3 phase circuit? What is the effect of load power factor on wattmeter readings?	6+4	3	2

Course Advisor: Manavi Sharma